

Lab Name

Zack Garza

Physics 210L

Effective Date of Report: March 25, 2014

Abstract—
THIS is a placeholder

CONTENTS

I	Theory	1
II	Methodology	2
III	Data	2
III-A	Linear Fit of V_R vs. i	2
III-B	Comparison of R_{Calc} and Resistance Box Values	2
III-C	Polynomial Fit of P_R vs. R_{Calc}	2

I. THEORY

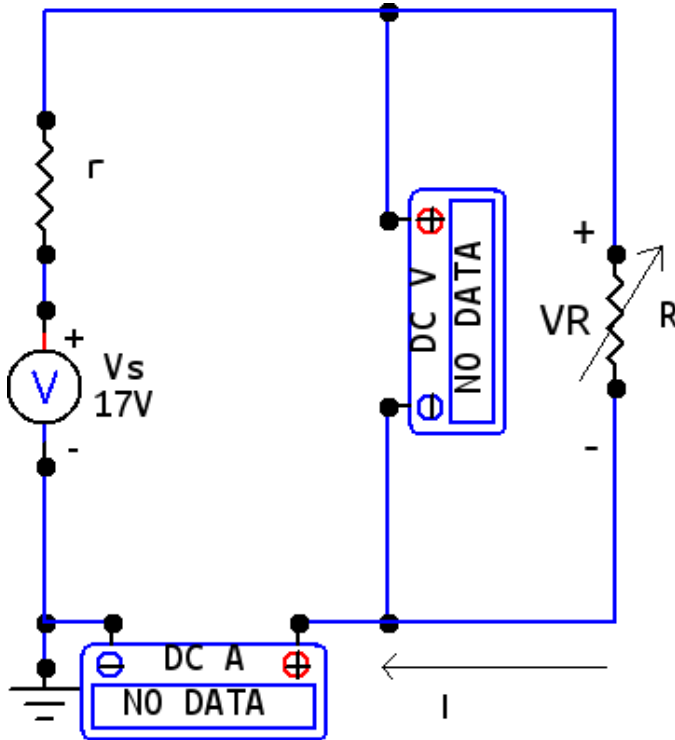


Figure 1. Diagram of circuit used in this experiment. R represents a variable load resistance, while r simulates the internal resistance of the power supply. I is the uniform current that flows through all three components of the circuit.

Kirchoff's Voltage Law states that the sum of the potential differences in a closed loop is equal to zero, such that

$$\sum V_{\text{Loop}} = 0.$$

For the circuit shown, the potential difference V_R across the load resistor can be found using this equation. Summing the voltages and rewriting them using $V = iR$ (according to Ohm's Law) yields

$$\begin{aligned}\epsilon - V_r - V_R &= 0 \Rightarrow \\ V_R &= \epsilon - V_r \Rightarrow \\ V_R &= \epsilon - ir\end{aligned}\quad (1)$$

where the current i is identical throughout the circuit, as its elements are wired in series, and r is the power supply's internal voltage.

The power released by the resistor R can also be expressed in terms of the known quantities ϵ , r , and R . From the power equation, it is known that $P = iV$. Because the current i is uniform everywhere, it can be related to the source voltage and the equivalent resistance of the entire circuit. Taking the source voltage to as ϵ and the equivalent resistance as $r + R$ and substituting it into the power equation yields

$$\begin{aligned}P &= iV, V = iR \Rightarrow P = \frac{i^2}{R} \Rightarrow \\ P_R &= \left(\frac{\epsilon}{r + R} \right)^2 R \Rightarrow \\ P_R &= \epsilon^2 \frac{R}{(r + R)^2}.\end{aligned}\quad (2)$$

Calculating the point at which maximum power transfer occurs requires taking the derivative of Equation 2 with respect to the load resistance. This results in

$$\frac{\partial P}{\partial R} = \epsilon^2 \left(\frac{(r + R^2) - 2R(R + r)}{(R + r)^4} \right).$$

Maximizing the power transferred to the load resistor requires setting this derivative equal to zero, which occurs when.

$$r + R^2 = 2R(R + r).$$

Solving this expression for R then forces the following condition to be true in order to maximize the power delivered to the load resistor R :

$$R = r.\quad (3)$$

II. METHODOLOGY

- 1) The circuit was constructed as shown in Figure 1, where r was a known resistor and R was a variable resistor box.
- 2) Digital voltmeters and ammeters were wired to measure V_R and i .
- 3) The power supply was set to 17.00 V, and its actual terminal voltage was measured.

- 4) The known resistor r was measured with an ohmmeter.
 - 5) The resistance of the variable load was incremented, and at each point data was taken for the voltage and current through R .
 - 6) Extra data points were taken at resistances approaching that of the known resistor.
-

III. DATA

$$r = .549 \text{ k}\Omega$$

$$\epsilon_{\text{Meas}} = 17.02 \text{ V}$$

A. *Linear Fit of V_R vs. i*

$$\text{Internal Resistance } r = (571 \pm 2)\Omega$$

$$\text{Source EMF } \mu_{\text{Theory}} = (16.99 \pm .04)\text{V}$$

$$\% \text{ Difference in } \epsilon = \underline{0.2\%}$$

$$\% \text{ Difference in } r = \underline{3.9\%}$$

B. *Comparison of R_{Calc} and Resistance Box Values*

Filler text.

C. *Polynomial Fit of P_R vs. R_{Calc}*

$$r = (573.2 \pm 0.7)\Omega$$

$$\% \text{ Difference} = \underline{0.38\%}$$

IV. ANALYSIS

- 1) *How can you determine the value for $R_{\text{Calculated}}$ that gives $P_{R\text{-Max}}$?*
- 2) *What are the possible discrepancies between the values of r obtained from the two function fits?*