

Lab 5: RC Circuits

Adam Olson, Nick Lonsdale, Zack Garza

April 4, 2014

Contents

1	Introduction	1
2	Theory	2
3	Equipment List	3
4	Methodology	4
4.1	Differentiator	4
4.2	Integrator	4
4.3	Low-Pass Filter	4
4.4	High-Pass Filter	4
4.5	Band-Pass Filter	4
5	Results	5
5.1	Differentiator	5
5.2	Integrator	5
5.3	Low-Pass Filter	5
5.4	High-Pass Filter	5
5.5	Band-Pass Filter	5
6	Appendicies	6
6.1	Derivations	6
6.2	Equipment Photographs	6
6.3	Circuit Diagrams	6
6.4	Circuit Photographs	6

Abstract

This is some abstract stuff.

Chapter 1

Introduction

This is an introduction.

Chapter 2

Theory

Chapter 3

Equipment List

1. Function Generator
2. Digital Oscilloscope (2 Channel)
3. Breadboard
4. Resistors;
 - (a) 1x 1.0 k Ω , ($\frac{1}{4}$ W)
 - (b) 2x 10.0 k Ω , ($\frac{1}{4}$ W)
5. Capacitors
 - (a) 1x .01 μ F
 - (b) 1x 100 pF
 - (c) 2x .001 μ F

Chapter 4

Methodology

4.1 Differentiator

4.2 Integrator

4.3 Low-Pass Filter

4.4 High-Pass Filter

4.5 Band-Pass Filter

Chapter 5

Results

5.1 Differentiator

5.2 Integrator

5.3 Low-Pass Filter

5.4 High-Pass Filter

5.5 Band-Pass Filter

Chapter 6

Appendices

6.1 Derivations

6.2 Equipment Photographs

6.3 Circuit Diagrams

6.4 Circuit Photographs

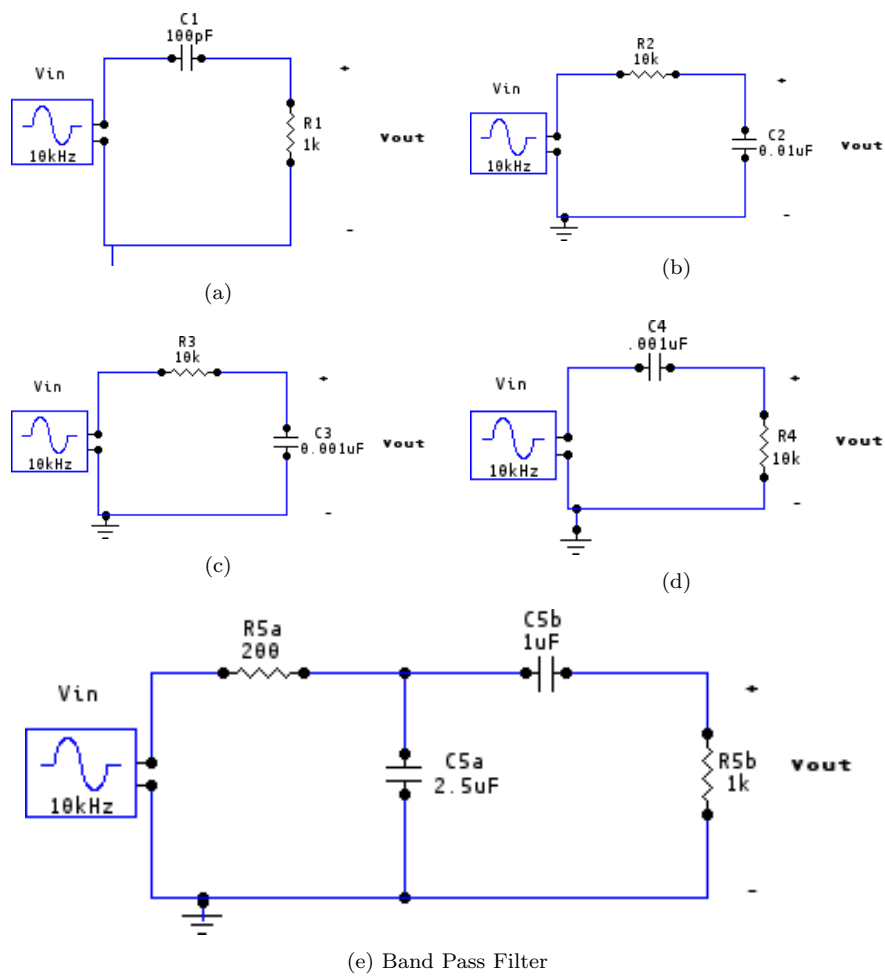


Figure 6.1: Circuit Diagrams