## 1

## Relationship Between Frequency and Impedance for a Series RLC Circuit

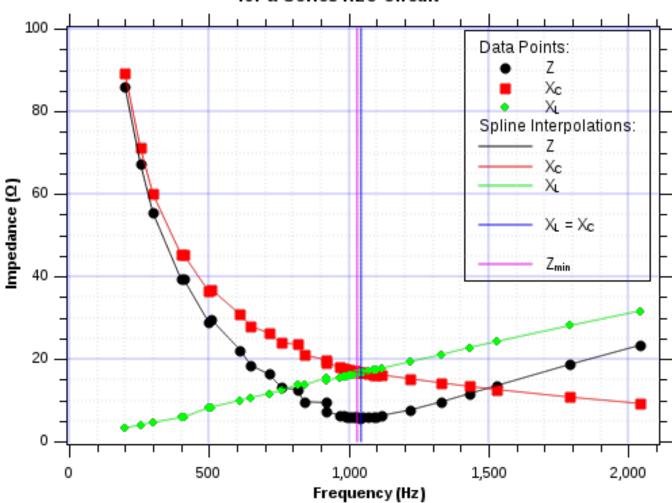


Figure 1. ?????

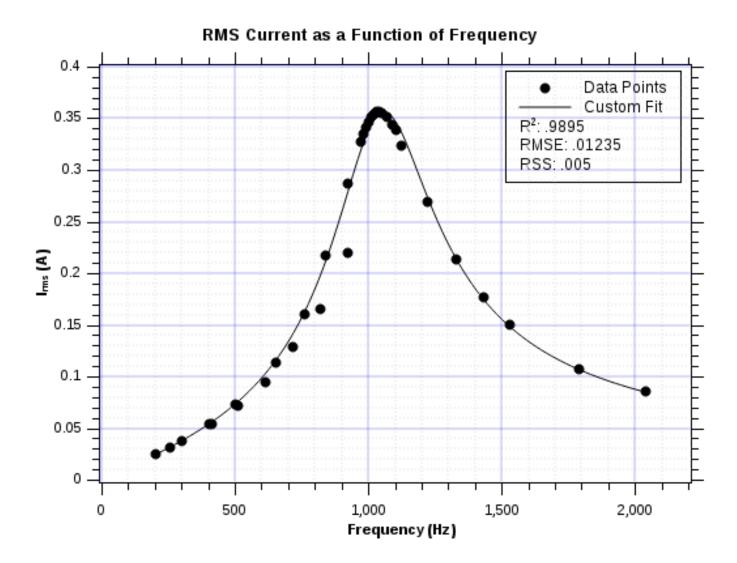


Figure 2. ?????

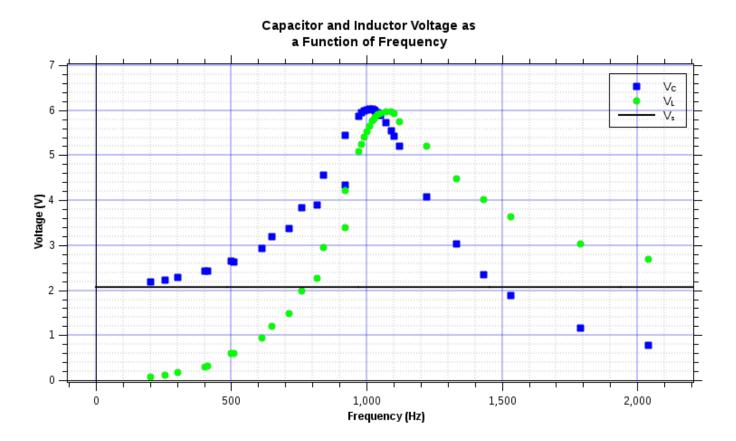


Figure 3. ?????

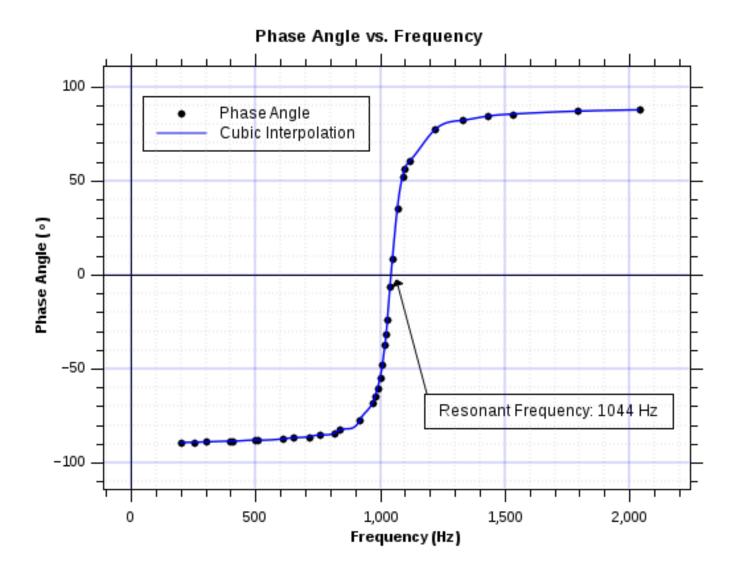


Figure 4. ?????

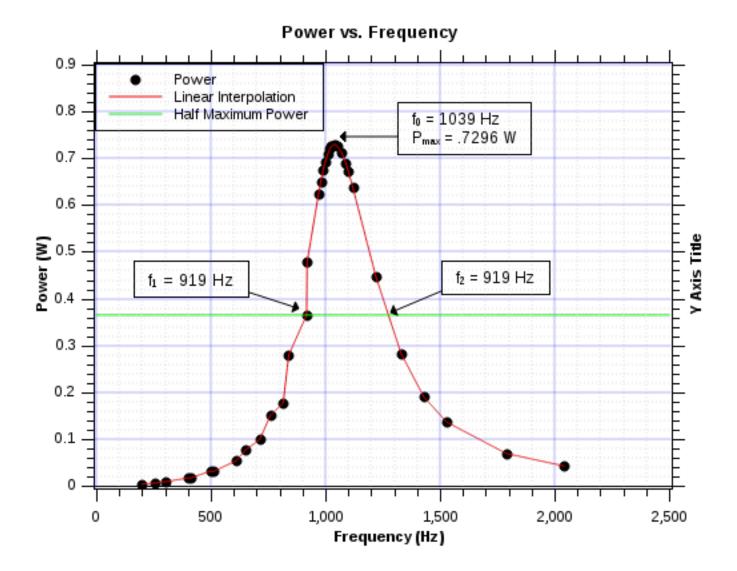


Figure 5. ?????