

RLC Circuits

Zack Garza

Physics 210L

Effective Date of Report: May 4, 2014

Abstract—

THE purpose of this experiment...

CONTENTS

I	Theory	1
II	Methodology	1
III	Results	1
III-A	Average Inductance/Capacitance Values	1
III-B	Impedance vs. Frequency	1
III-C	Current vs. Frequency	1
III-D	Difference between measured and fitted values	2
III-E	Theoretical Resonant Frequency	2
III-F	Voltage vs Frequency	2
III-G	Phase Angle vs. Frequency	2
III-H	Power vs. Frequency	2
III-I	Quality Factor	2
IV	Analysis and Conclusion	2

I. THEORY

The following expressions were used in the analysis of this circuit:

$$\begin{aligned}\omega &= 2\pi f \\ \omega_0 &= \sqrt{\frac{1}{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \\ X_L &= \frac{V_L}{I} \\ X_C &= \frac{V_C}{I} \\ Z &= \frac{V_s}{I} \\ L &= \frac{X_L}{2\pi f} \\ C &= \frac{1}{2\pi f X_C} \\ \theta &= 360^\circ f \Delta t \\ P &= I_{\text{rms}} V_{\text{rms}} \cos \theta \\ Q &= \frac{\omega_0 L}{R} \\ Q &= \frac{f_0}{\Delta f} = \frac{\omega_0}{\Delta \omega}\end{aligned}$$

Δf is the width of the resonance peak between the points where $V = \frac{1}{\sqrt{2}} V_{\text{max}}$

II. METHODOLOGY

- 1) A simple RLC series circuit was constructed. DMMs were wired to measure ΔV_L , and ΔV_C , the voltages of the inductor L and the capacitor C respectively.
- 2) An ammeter was wired in series with the previous elements to measure I , and an oscilloscope was wired to measure ΔV_s and ΔV_R , the voltages across the source and the resistor R respectively.
- 3) The resistance of R was measured in order to determine phase difference between the source voltage V_s and the current I . Δt between these two signals was recorded.
- 4) The potential difference of the supply was set to a constant 2.0 V (rms), and the ammeter was set to the 430 mA scale.
- 5) The expected resonance frequency f_0 was calculated, and a range of frequencies symmetric about f_0 were chosen for measurement.
- 6) For each frequency f , the following quantities were measured:
 - a) I_{rms}
 - b) V_L
 - c) V_C

Extra data points were taken at frequencies approaching f_0 .

- 7) The data was then placed into a spreadsheet to calculate various variables, which were used in the analysis section.

III. RESULTS

A. Average Inductance/Capacitance Values

$$\begin{aligned}\bar{L} &= n \pm d \\ \bar{C} &= n \pm d\end{aligned}$$

B. Impedance vs. Frequency

$$\begin{aligned}Z_{\text{min}} &= n \Omega \\ f_{\text{res, meas}} &= n \text{ Hz}\end{aligned}$$

Why is R_{meas} not the same as the value of the resistor used in the circuit?

C. Current vs. Frequency

The data was fitted to the function

$$I_{\text{rms}} = \frac{V_{\text{rms}} \omega}{\sqrt{(R\omega)^2 + L^2(\omega^2 - \omega_0^2)^2}} \quad (1)$$

$$\frac{R_{\text{fit}} = n\Omega}{f_{\text{res, fit}} = n \text{ Hz}}$$

D. Difference between measured and fitted values

What is the percent difference between R (measured) and R (fit)? Is R (measured) within the uncertainty of R (fit)?

Percent Difference: $x\%$

E. Theoretical Resonant Frequency

The resonant frequency, calculated from the mean values of L and C from step 1 is given by

$$f_{\text{res,theor}} = \frac{1}{2\pi\sqrt{L_{\text{avg}}C_{\text{avg}}}}. \quad (2)$$

$$\Rightarrow f_{\text{res,theor}} = n\text{Hz}$$

Comparing this to the values determined in Steps 2 and 3 above, we have

% Difference, Step 2: $x\%$

% Difference, Step 3: $x\%$

F. Voltage vs Frequency

What does this graph tell you?

G. Phase Angle vs. Frequency

Does this curve agree with theory? Explain.

H. Power vs. Frequency

$\Delta f = x \text{ Hz}$

I. Quality Factor

The calculated quality factor is given by

$$Q_{\text{calc}} = \frac{f_{\text{max, meas}}}{\Delta f} \quad (3)$$

Calculated Quality Factor: $Q_{\text{calc}} = x \pm d$

The theoretical Quality factor is given by

$$Q = \frac{\omega_0 L}{R_{\text{meas}}}, \quad (4)$$

where ω_0 is given by $2\pi f_{\text{res, meas}}$ from Step 2 and L is L_{avg} from Step 1.

Theoretical Quality Factor: $Q = x \pm d$

IV. ANALYSIS AND CONCLUSION